
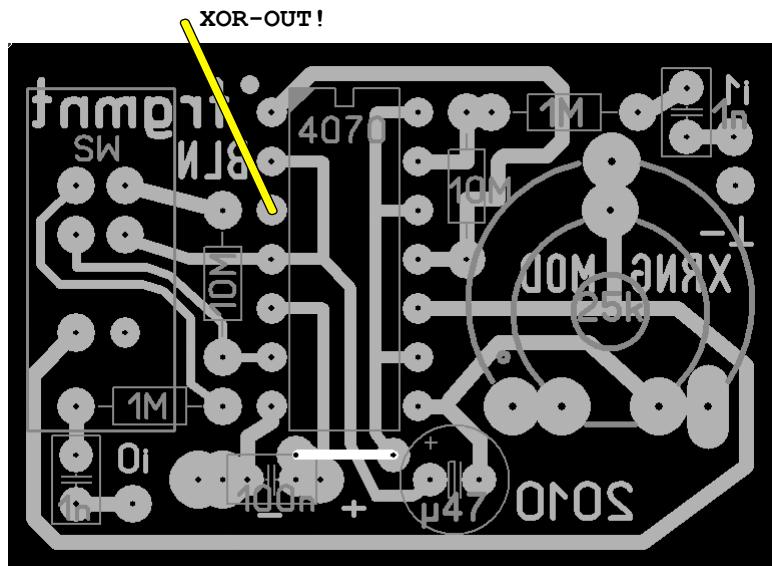


Spectroscopy Workshop

CTM.10 OVERLAP 01-06.02.2010

XOR

Modulator

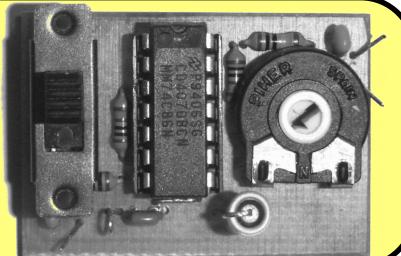

4011 Quad NAND


NAND

A	B	$A \oplus B$
0	0	1
0	1	1
1	0	1
1	1	0

4011



+V inverts the Input
GND looks Table

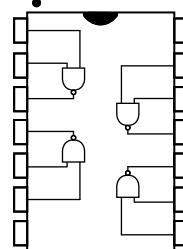

4077 Quad XNOR



XNOR

A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

4077



GND inverts
+V does not invert

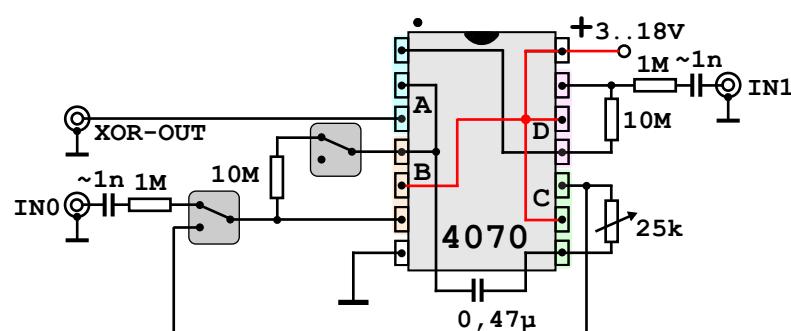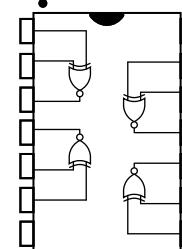

4070 Quad XOR



XOR

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

4070



+V inverts the Input
GND does not invert

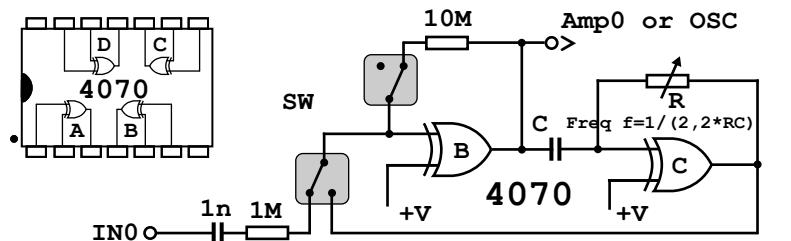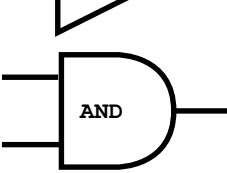

XOR RNG MOD


CTM, Berlin, D
tob.de.vu / 2010
X Objct Bhvirs

Switch States: 2 x XOR-Oscillator
1 x XOR-Amp / 1 x XOR off

->Features: 1 Internal Oscillator
1 or 2 Inputs with "Amps"



+V inverts the Input
GND does not invert

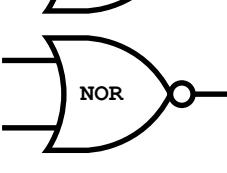

+V inverts the Input
GND does not invert









XOR

XNOR

Creative Commons


BY NC SA 3.0 German

INV Amplifier

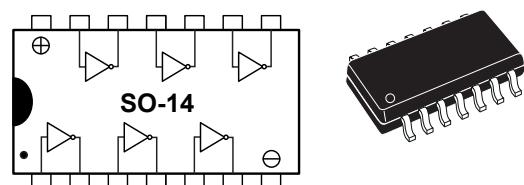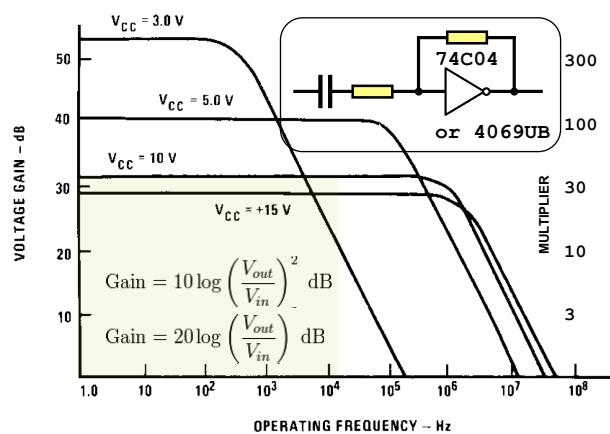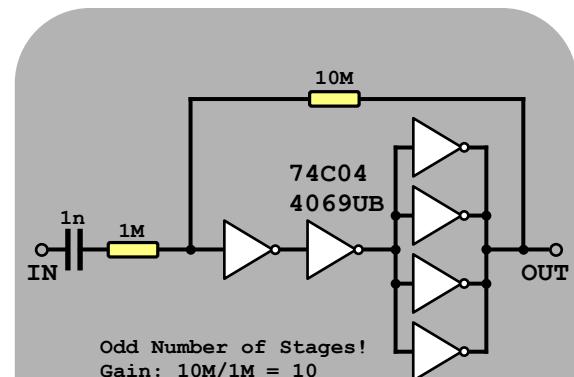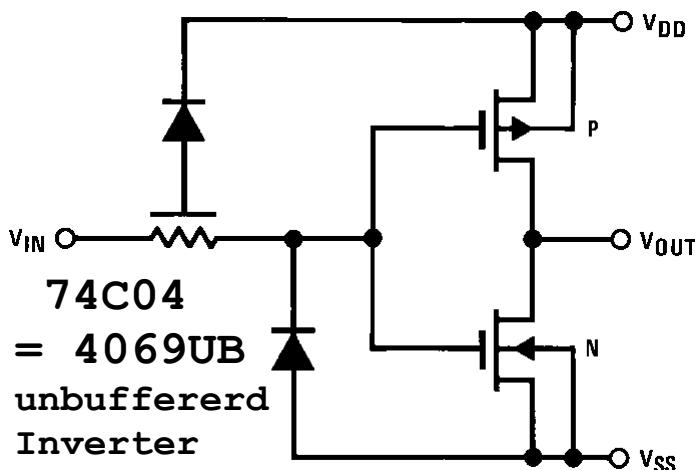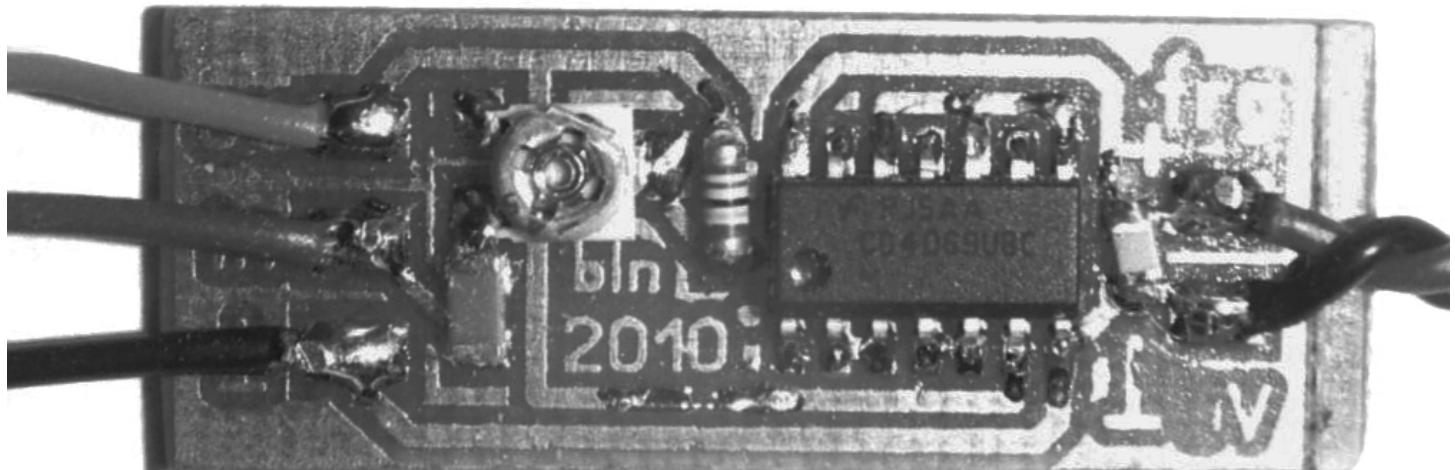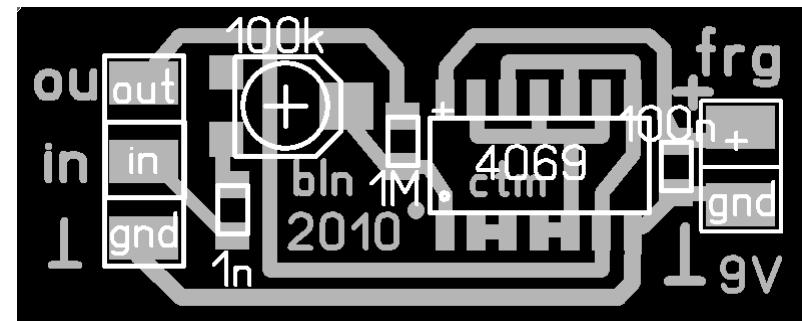


INF Amp SMD
 CTM, Berlin, D
tob.de.vu / 2010
 x Objct Bhvirs

FET-PreAmp SMD 2010

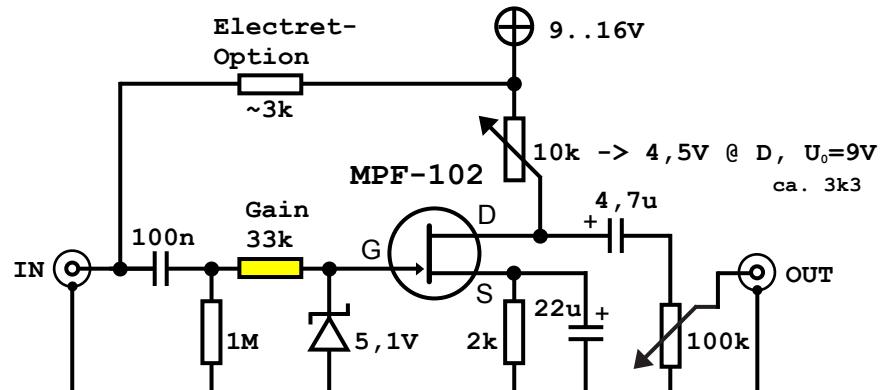


Some schematic,
just a different Style:

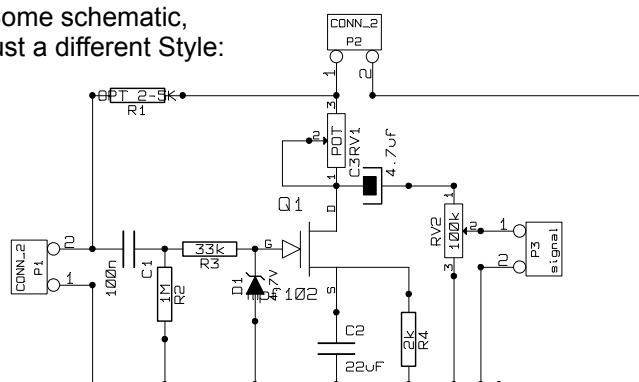

```

1 x 10..22k lin Pot
1 x 100k lin Pot
1 x 2k = 2 x 1k
1 x 33k
1 x 1M
1 x 4u7 Elco
1 x 22uF Elco
1 x MPF 102 FET
1 x 5V1 Zener diode
1 x PCB single sided

```

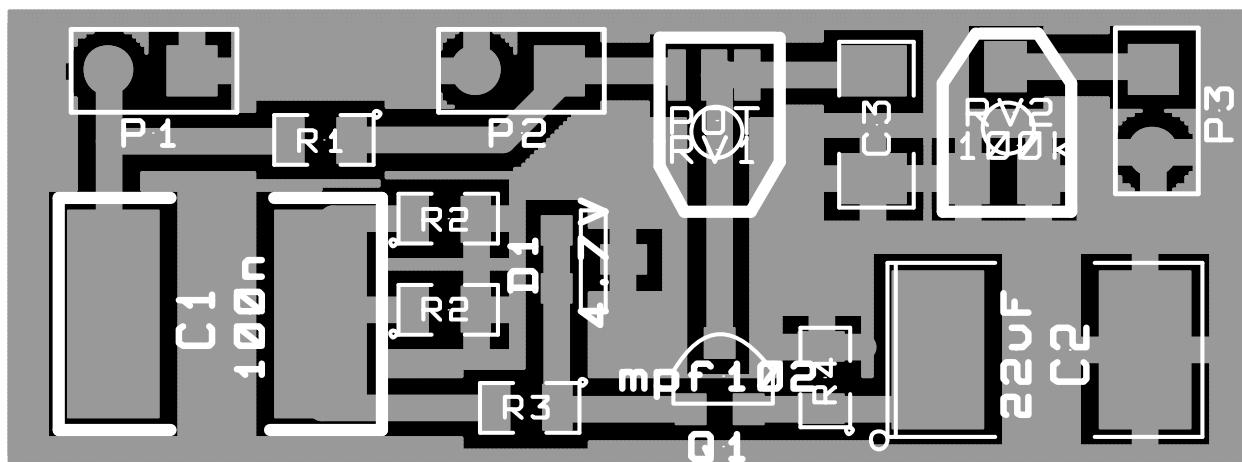

0	1	2	3	4	5	6	7	8	9
BK LA	BR OW	RE D	OR AG	YE LW	GN RE	BL UE	VI OL	GY RE	WH IT





FET-PreAmp SMD 2010
PRELIMINARY GRAPH for CTM, Berlin
tob.de.vu / 2010
Transmitting Object Behaviors



Creative Commons License: BY-NC-SA v3.0 Germany

VLF-Detector

Very Low Frequency

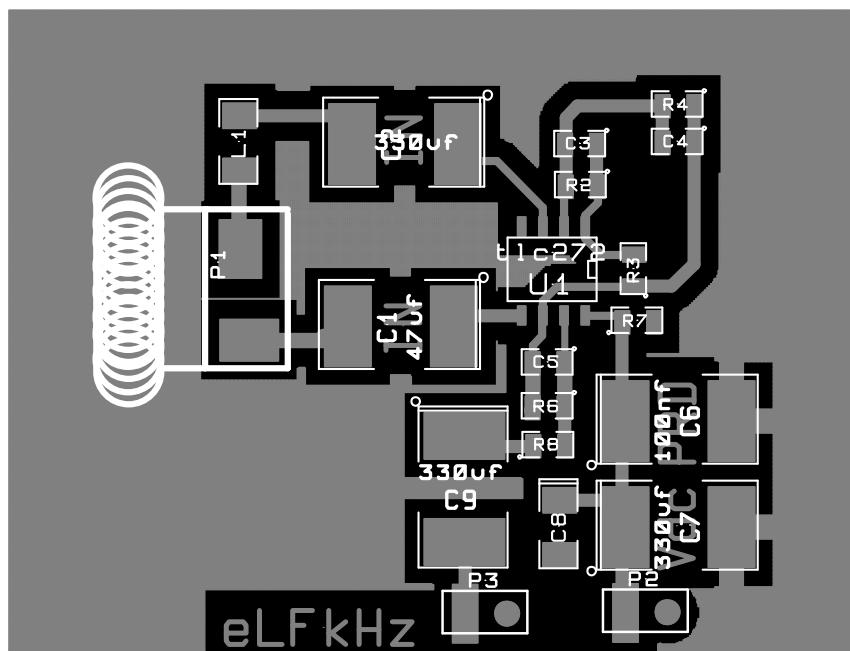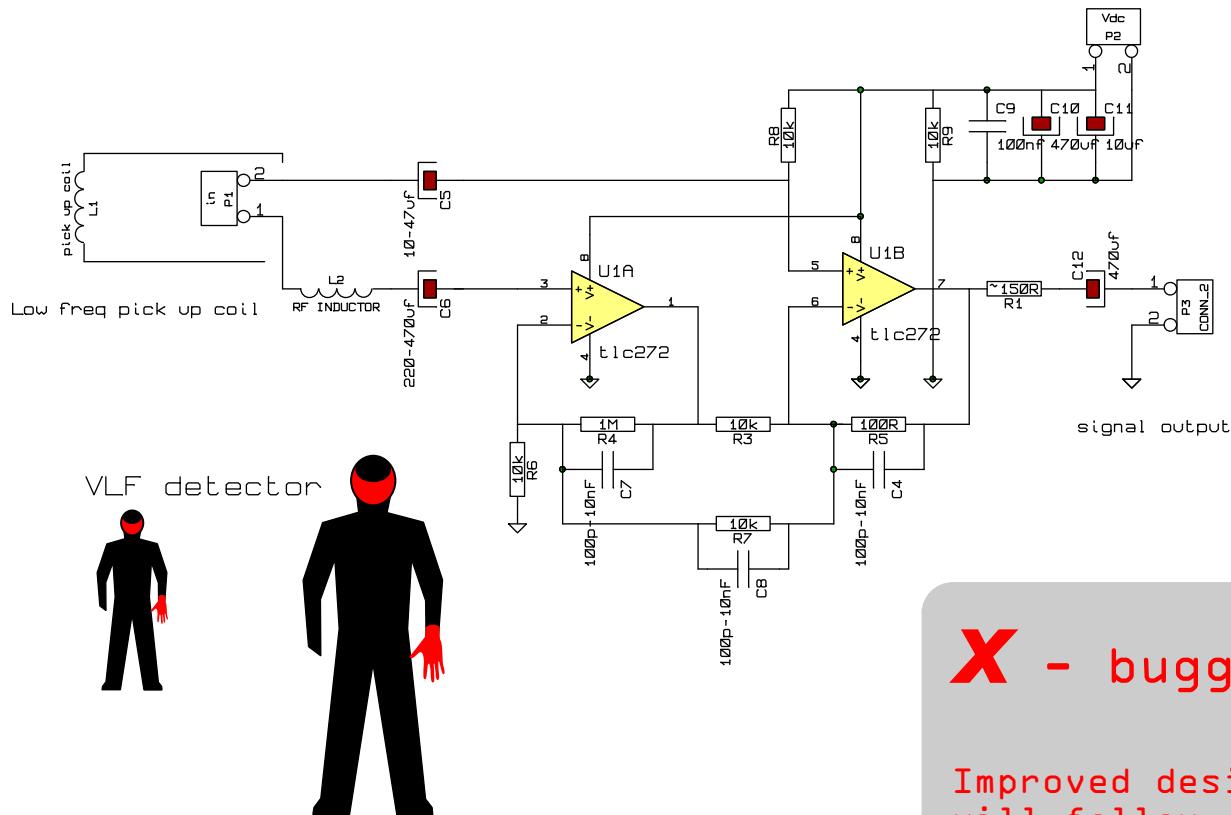

0	1	2	3	4	5	6	7	8	9
BK LA	BR OW	RE D	OR AG	YE LW	GN RE	BL UE	VI OL	GY RE	WH IT



VLF-Detector SMD 2010
PRELIMINARY GRAPH for CTM, Berlin
tob.de.vu / 2010
Transmitting Object Behaviors




OPTO



Amplification of Photocurrent

Device Type	Type	Light Current			Dark Current			Power Diss. mW
		min. mA	max. mA	@ V	max. nA	@ V		
TIL99	As Phototransistor	1	—	5	100	10	250	
	As Photodiode	40* μ A typ	—	0-50	10	10	250	




4049UB oldschool Inverter

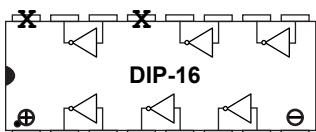

74HC14 etc SchmittTrigger

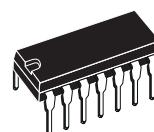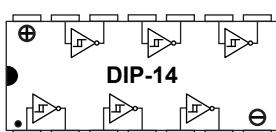

From **BPW40** datasheet:

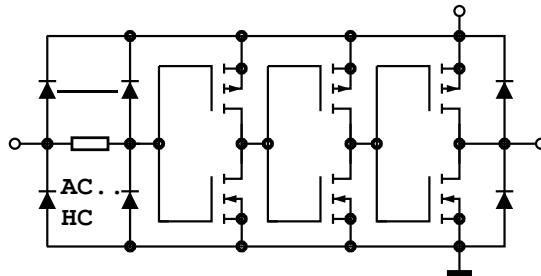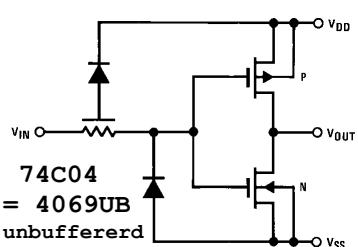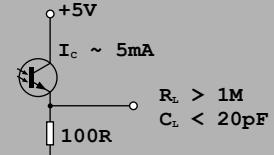


Photodiode:

Under forward bias, conventional current will pass from the anode to the cathode, following the arrow in the symbol. Photocurrent flows in the opposite direction.

Unwanted photodiodes



Since transistors and ICs are made of semiconductors, and contain P-N junctions, almost every active component is potentially a photodiode. Many components, especially those sensitive to small currents, will not work correctly if illuminated, due to the induced photocurrents. In most components this is ***not desired***, so they are placed in an opaque housing. Since housings are not completely opaque to X-rays or other high energy radiation, these can still cause many ICs to ***malfuction*** due to induced photo-currents.

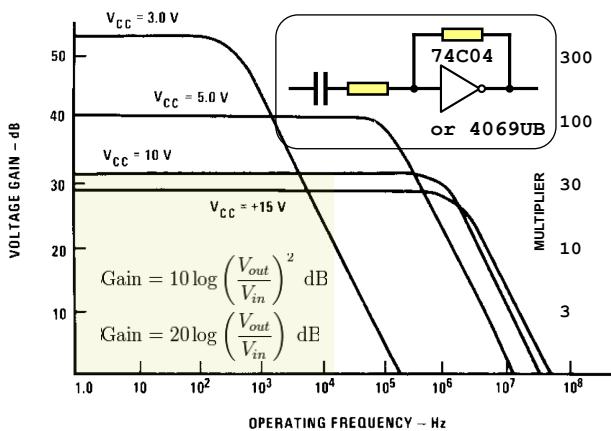


Single Supply OpAmp Buffer Circuit

Improved Replacement for TLC272, TLC277


Rail-To-Rail Input

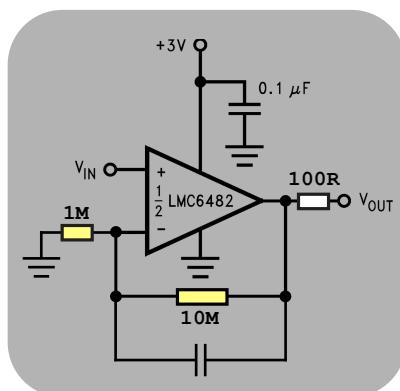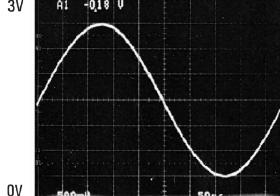

Rail-To-Rail Output

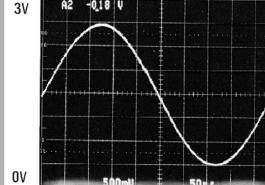



TS912 Rail-to-Rail OpAmp

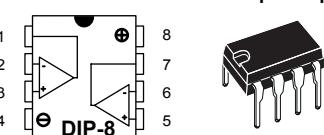

Optical Receiver

EXTERNAL SIGNAL
MODULATION INPUT

OPTICAL RECEIVER

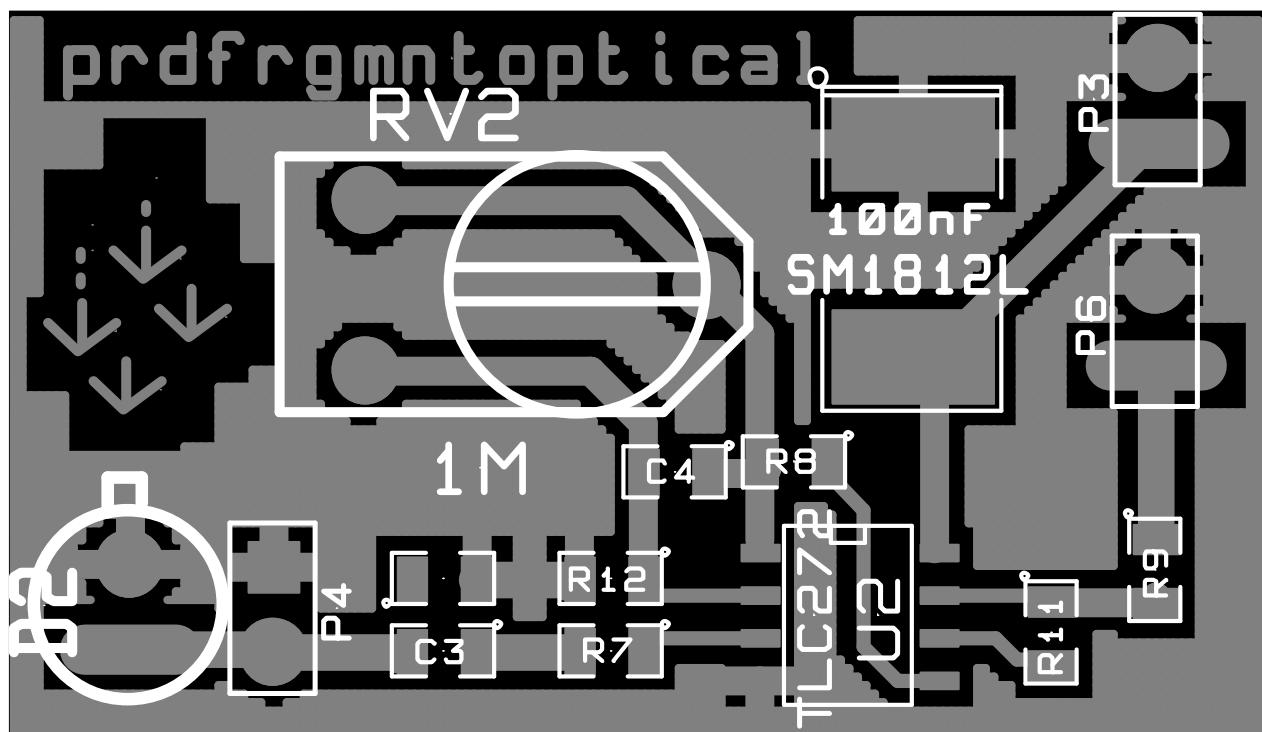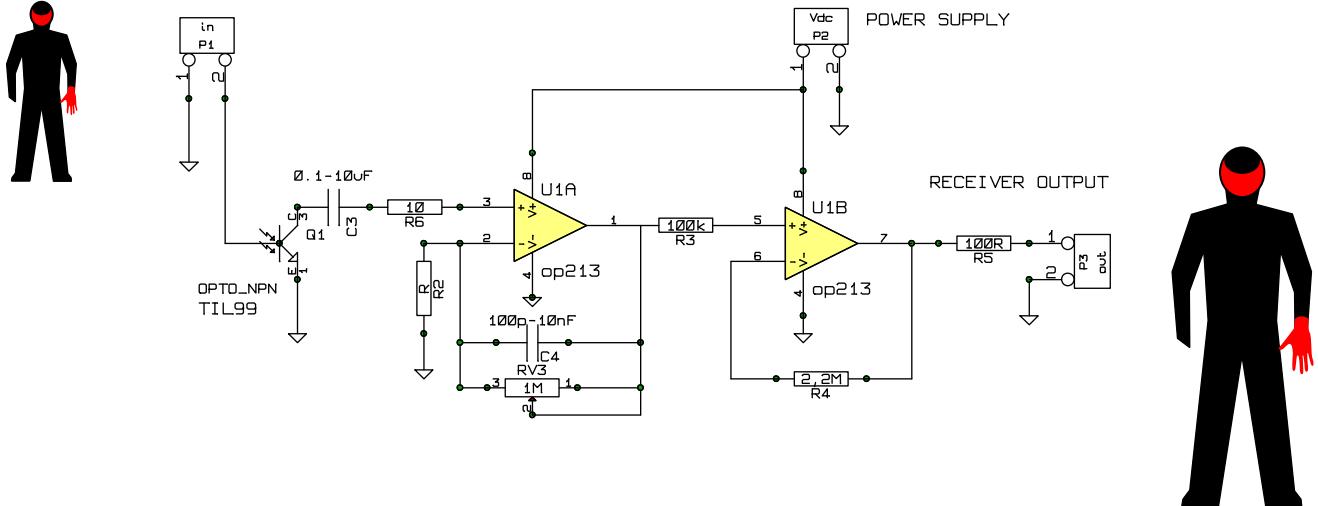

0	1	2	3	4	5	6	7	8	9
BK	BR	RE	OR	YE	GN	BL	VI	GY	WH

LA OW D AG LW RE UE OL RE IT




Optical Receiver SMD 2010
PRELIMINARY GRAPH for CTM, Berlin
tob.de.vu / 2010
Transmitting Object Behaviors



Creative Commons License: BY-NC-SA v3.0 Germany


Ultrasonic Detector

30..60 kHz FAULTY Design

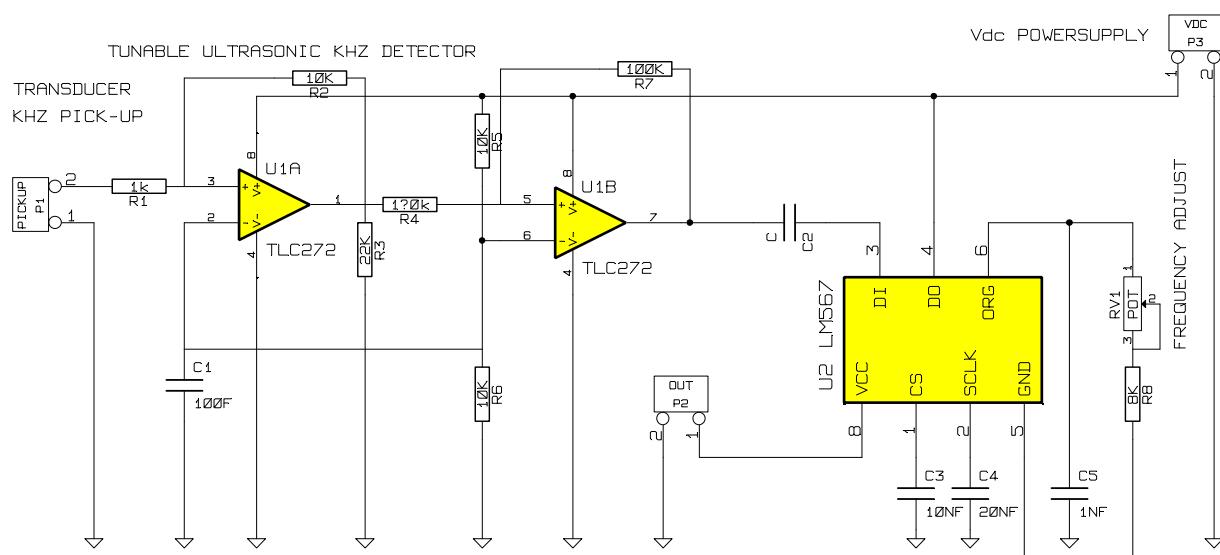


C1 100nF
C2 C SM0805
C3 10NF
C4 20NF
C5 1NF output
P1 PICKUP / ultrasonic transducer
P2 OUT
P3 VDC powersupply
R1 1k
R2 10K
R3 22K
R4 1?0k
R5 10K
R6 10K
R7 100K
R8 8K
RV1 POT
U1 TLC272
U2 LM567

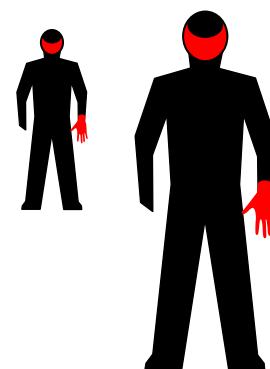R Resistor [Ohm] **C** Capacitor [Farad]
U Integrated circuit **P** Pin/Plug



X - buggy!

Improved design will follow.

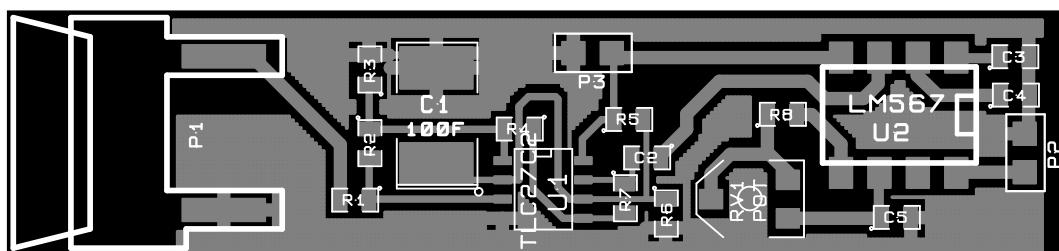

0	1	2	3	4	5	6	7	8	9
BK	BR	RE	OR	YE	GN	BL	VI	GY	WH

LA OW D AG LW RE RE UE OL RE IT





Ultrasonic Det SMD 2010
PRELIMINARY GRAPH for CTM, Berlin
tob.de.vu / 2010
Transmitting Object Behaviors



386 PwrAmp SMD 2010

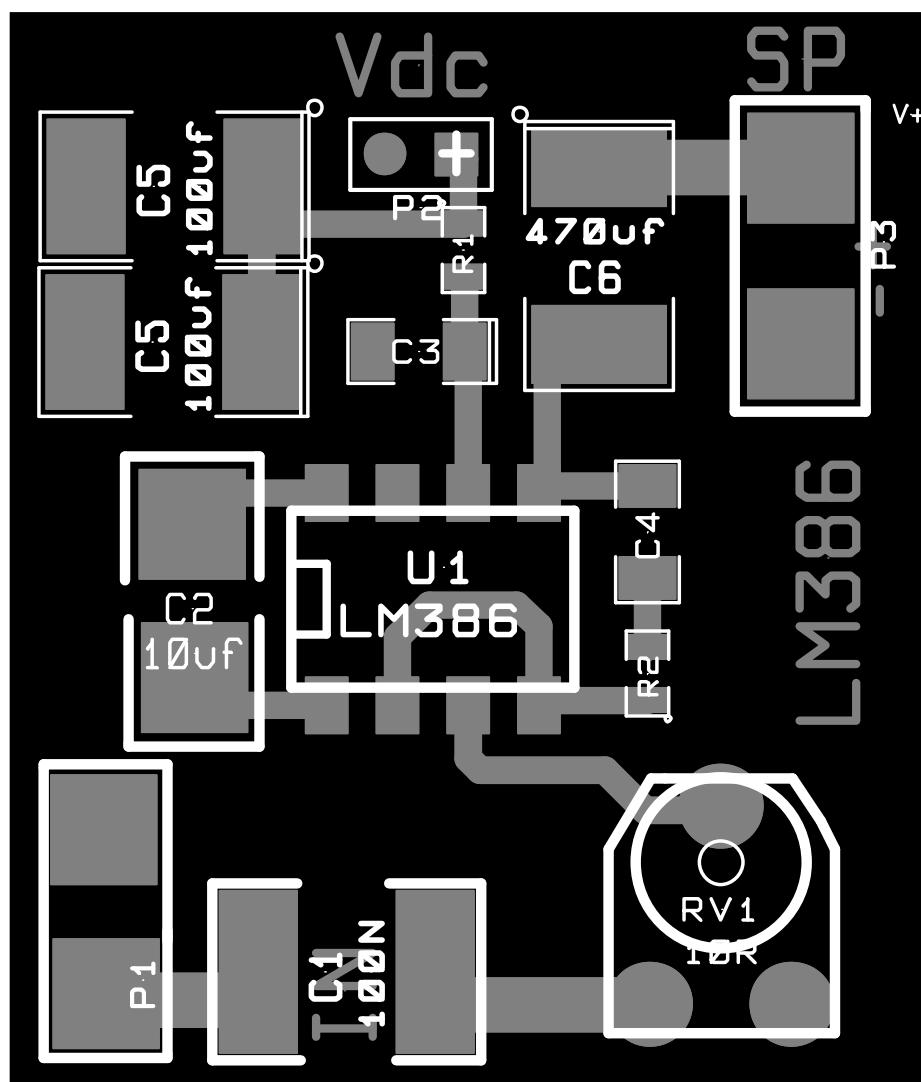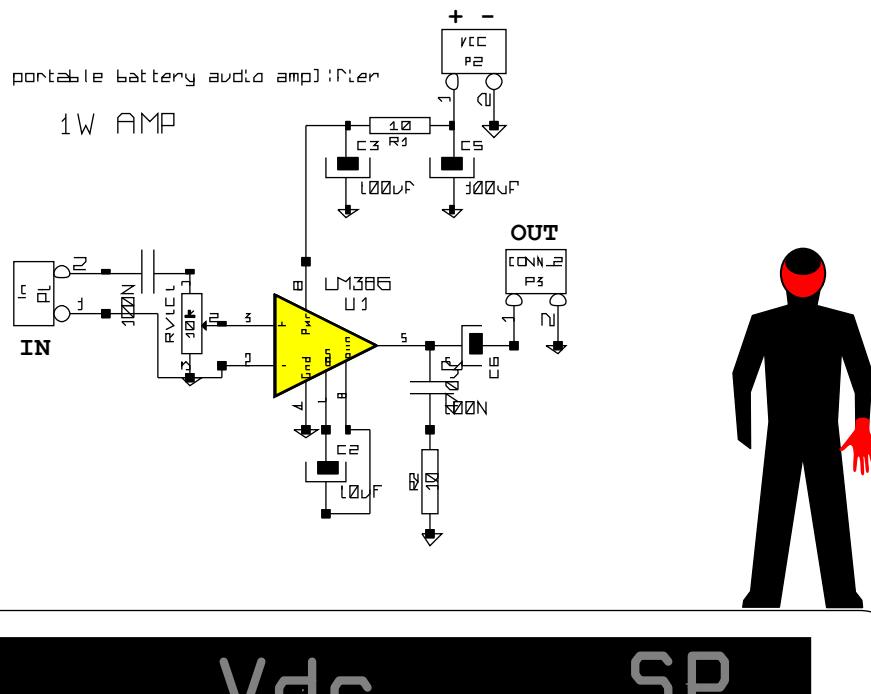1 * LM 386
 1 * 10k Poti
 2 * 10R
 2 * 100n Ceramic Cap
 1 * 10 μ ElCap
 2 * 100 μ ElCap
 1 * 470 μ F ElCap



0	1	2	3	4	5	6	7	8	9
BK	BR	RE	OR	YE	GN	BL	VI	GY	WH

BK BR RE OR YE GN BL VI GY WH
 LA OW D AG LW RE UE OL RE IT





386 PwrAmp SMD 2010
 PRELIMINARY GRAPH for CTM, Berlin
 tob.de.vu / 2010
 Transmitting Object Behaviors



fm-tRANS

Alternative Design

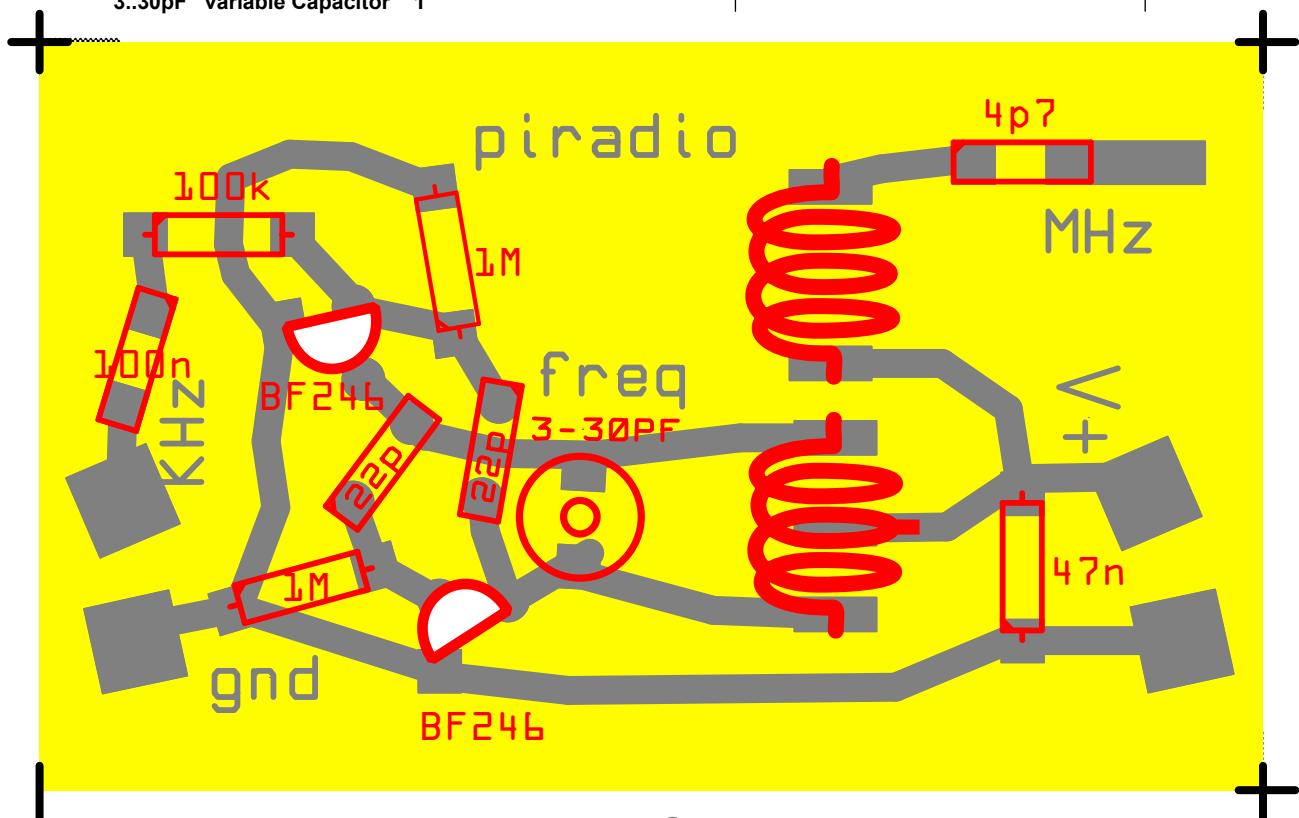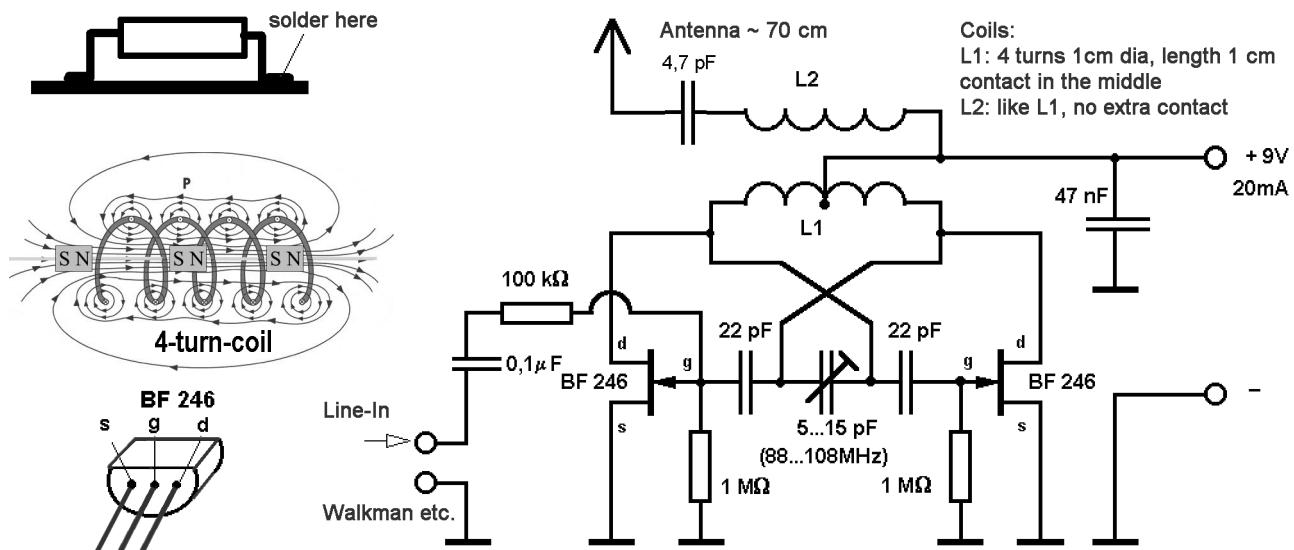



fm-tRANS 2010

PRELIMINARY GRAPH for CTM Berlin, D
Jo frgmt Grys / tob.de.vu / 2010
Transmitting Object Behaviors



Creative Commons License: BY-NC-SA v3.0 German

fm-tRANS

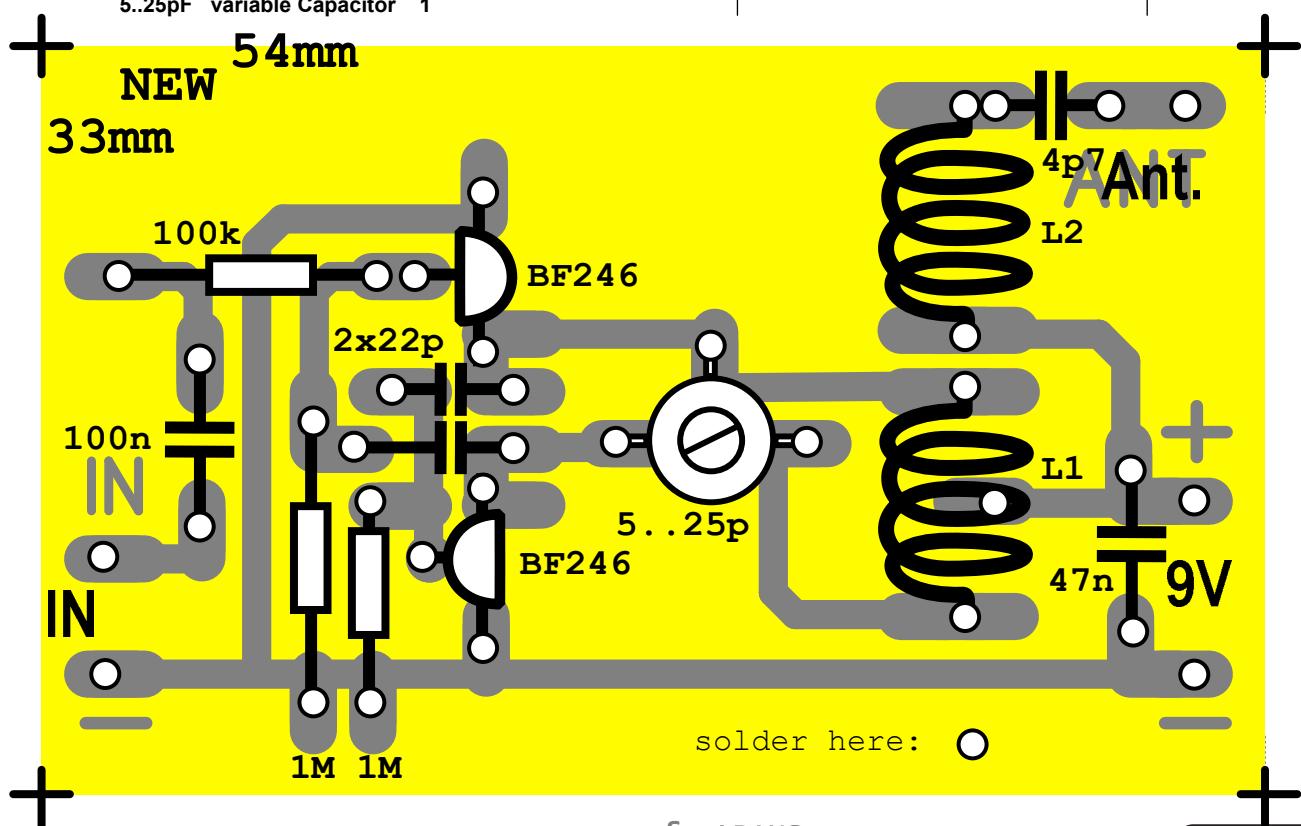
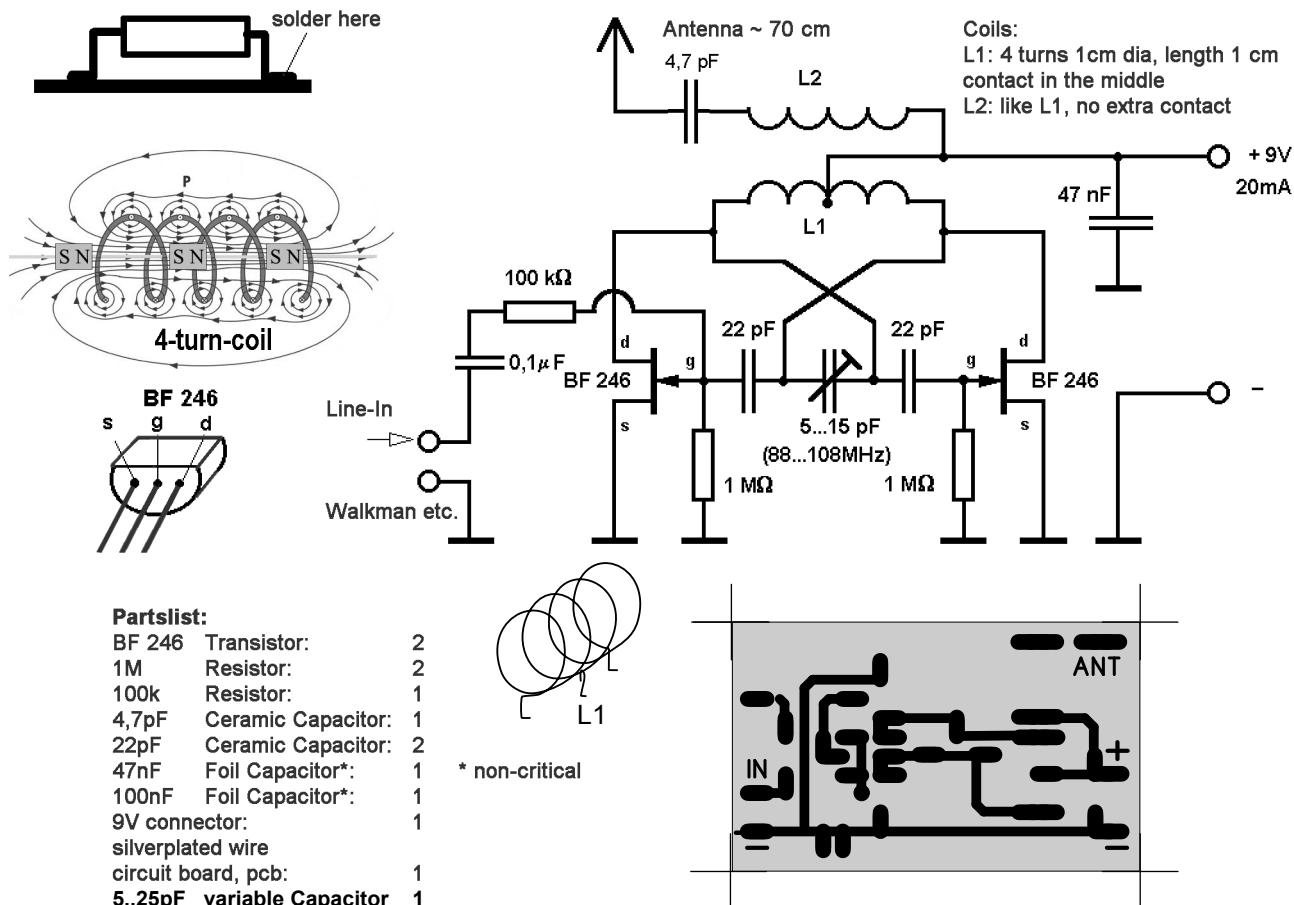


fm-tRANS


PRELIMINARY GRAPH AFTER PIKSEL, Bergen
 Jo frgmnnt Grys / tob.de.vu / 2008
 Transmitting Object Behaviors



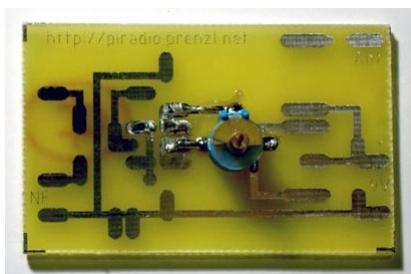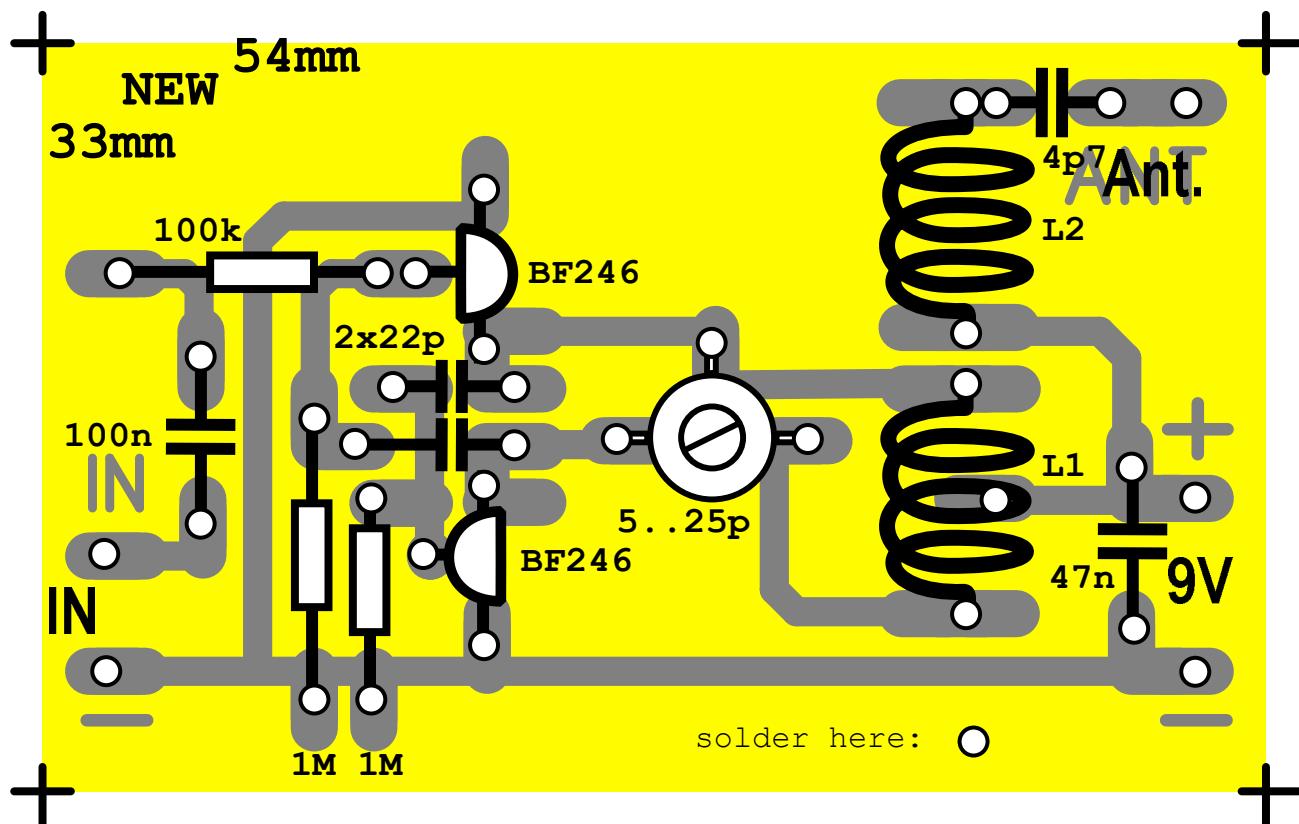Creative Commons License: BY-NC-SA v3.0 German



Add the varicap

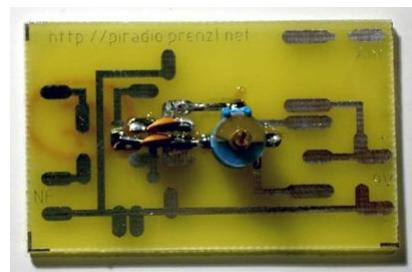

Add two 22p capacitors



Add two transistors



Add two 1M resistors



Add the 100n capacitor



Add the 100k resistor



Add two coils & mid connection



Add the 47n capacitor



Connect both channels, battery- & 70cm of antenna-cable

TIPS: The coils are easily fabricated by winding the silverwire around a 10mm drill bit.. When finished & powered, tune a radio to a noisy space between stations, then tune the transmitter by slowly turning the screw of the varicap with a non-metallic screwdriver until the noise stops. Now you can snip against the coils & tune to a clear radio sound! Increase stability: Use stabilized power for long term frequency stability. Connect rear copper plane to ground. Extend range: With a tuned dipole antenna & strong input signal.